

INDIAN INSTITUTE OF TECHNOLOGY BOMBAY
ELECTRICAL ENGINEERING DEPARTMENT

EE-Quiz 2

Friday May 12, 2023
 Time: 08:15-09:00

MS-101 Makerspace
 Spring Semester 2022-23

Marks: 40
 (To be re-scaled)

Roll Number: _____ **Name:** _____

Division: _____ **Batch:** _____ **Signature:** _____


Q	1	2	3	4	5	6	Total
Marks							

This question paper has 4 pages containing 6 questions. Answer these in the space provided with the questions.

Steps for arriving at numerical answers must be shown.

Numerical answers must be accurate to within 0.1%

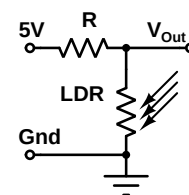Q-1 We use a circuit as shown on the right to detect light using a light dependent resistor (LDR). The resistance of LDR in dark is $100\text{ k}\Omega$. Its resistance when exposed to the brightest light to be measured is $5\text{ k}\Omega$.




- a) What should be the value of the series resistor R such that the output voltage V_{Out} is 2.0 V in dark?

Steps:

Answer: _____

 – [2]

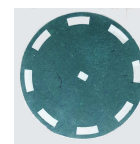- b) If we use a $25\text{ k}\Omega$ resistor for R and a rotating wheel with slots to periodically interrupt the brightest light (for which the LDR resistance is $5\text{ k}\Omega$), what will be the peak to peak voltage at the output (V_{Out})?



Steps:

Answer: _____

 – [4]

- c) The rotating wheel used to chop light has 8 slots with equal spacing as shown in part b) above. If the wheel rotates at a constant speed of 150 revolutions per minute, what will be the time period of the periodic signal observed at V_{Out} ?
Steps:

Answer: _____

 – [3]

– [Q1: 2 + 4 + 3 = 9 marks]

Q–2 The voltage output from a sensor ranges between 0 V and 2.0 V. This is to be measured using the in-built 10 bit ADC in Arduino. To maximize resolution of the measurement, we want to use an externally supplied reference voltage of 2.0 V to the ADC.

- a) To which pin of Arduino should we connect the reference voltage of 2.0 V?

Answer: _____

 – [2]

- b) Which library function should we call and with what argument, so that this reference voltage is used for A to D conversion?

Answer: _____

 – [2]

- c) What precaution should we take while writing a sketch using an external reference voltage?

Answer:

– [3]

– [Q2: 2 + 2 + 3 = 7 marks]

Q–3 We want to construct a toy car controlled by an Arduino board which can carry out the following four commands:

- i) **F** (Move Forward), ii) **B** (Move backwards), iii) **R** (Turn right) and iv) **L** (Turn Left).

Rather than using 4 port pins from Arduino, we want to use just two port pins (D2 and D3) and generate the four commands by decoding the outputs using a digital logic circuit.

The commands are encoded as shown in the table on the right

D2	D3	Command
0	0	F : Forward
0	1	B : Backwards
1	0	R : Turn Right
1	1	L : Turn Left

- a) Express each of these commands as a logic function of D2, D3 and their complements.

Answer: Fill in the logic function in the table below:

Command	Logic Function
F : Forward	=
B : Backwards	=
R : Turn Right	=
L : Turn Left	=

– [2]

- b) We want to generate the decoded commands **F**, **B**, **R** and **L** as positive TRUE signals derived from the digital outputs at pins D2 and D3 using **no more than 2 inverters and four 2-input NOR gates** for decoding all commands.

Provide a logic diagram for decoding the four commands from the two digital values (D2 and D3) with this constraint.

Answer:

– [4]

– [Q3: 2 + 4 = 6 marks]

Q-4 What will be the value returned by the library function “map” if it is called as: `map(95, 50, 1000, 0, 250)`?

You must provide the steps used for calculating your answer.

Steps:

Answer: _____

– [Q4: 4 marks]

Q-5 The library function “attachInterrupt()” is used for setting up interrupts in an Arduino card. Consider a call to this function as:

`attachInterrupt(digitalPinToInterrupt(2), handler, CHANGE);`

Subsequent to executing this call,

a) What kind of signal will result in an interrupt?

Answer: _____

– [2]

b) On which pin should this signal occur in order to cause an interrupt?

Answer: _____

– [2]

c) Which function will be run when an interrupt occurs? Specify its return and argument types.

Answer: _____

– [4]

– [Q5: 2 + 2 + 4 = 8 marks]

Q–6 Arduino library provides two functions for measuring pulse width: “pulseIn()” and “pulseInLong()”.

a) Why should interrupts be disabled for an accurate measurement of pulse width if we use the function “pulseIn()”?

Answer:

– [3]

b) Why should interrupts be enabled if we use the function “pulseInLong()” for pulse width measurement?

Answer:

– [3]

– [Q6: 3 + 3 = 6 marks]

Paper Ends
