

MS101 – Makerspace
2023-24/I (Autumn Semester)
EE Quiz - 1 (Aug 23, 2023 Wed)

Answers to Numerical Questions

Ques.	Answers	Comments
1	FALSE	
2	250 Ω	
3	96 mA	
4	$V_{AB} = -3V, I_L = -1 \text{ mA}$	
5	2.6 mA	
6	17 V	
7	9	
8	B	
9	A, B	
10	$A_v = -0.5, A_i = -500, A_p = 250$, Yes	
11	$R = R1 = 100 \text{ k}\Omega, R_{in} = 0 \Omega$	
12	$A_{v1} = 6, R_{in1} = 20 \text{ k}\Omega, A_{v3} = -10, R_{in3} = 10 \text{ k} \Omega$	